

Digital Logic Appendix A

Boolean Algebra
Gates
Combinatorial Circuits
Sequential Circuits

19.9.2000 Copyright Teemu Kerola 2000 1

Boolean Algebra

- George Boole
 - ideas 1854
- Claude Shannon,
 - apply to circuit design, 1938 (piirisuunnittelu)
- Describe digital circuitry function
 - programming language?
- Optimise given circuitry
 - use algebra (Boolean algebra) to manipulate (Boolean) expressions into simpler expressions

19.9.2000 Copyright Teemu Kerola 2000 2

Boolean Algebra

- Variables: A, B, C
- Values: TRUE (1), FALSE (0)
- Basic logical operations:
 - binary: AND (•), OR (+) $A \bullet B = AB$ $B + C$
 - unary: NOT () \bar{A} (ja, tai, ei)
- Composite operations, equations
 - precedence: NOT, AND, OR
 - parenthesis $D = A + \bar{B} \bullet C = A + ((\bar{B})C)$

19.9.2000 Copyright Teemu Kerola 2000 3

Boolean Algebra

- Other operations
 - NAND $A \text{ NAND } B = \text{NOT}(A \text{ AND } B) = \overline{AB}$
 - NOR $A \text{ NOR } B = \text{NOT}(A \text{ OR } B) = \overline{A + B}$
- Truth tables
 - What is the result of the operation?

Table A.1

		Q	
	AND	0	1
P	0	0	0
	1	0	1

19.9.2000 Copyright Teemu Kerola 2000 4

Postulates, Identities in Boolean Algebra

- How can I manipulate expressions?
 - Simple set of rules?
- Basic identities (Table A.2)
 - commutative laws (vaihdantalait)
 - distributive laws (osittelulait)
 - identity elements (identiteetit)
 - inverse elements (vasta-alkiot)
 - associative laws (liitántälait)
 - DeMorgan's theorem (DeMorganin laki)

19.9.2000 Copyright Teemu Kerola 2000 5

Gates (portit)

- Fundamental building blocks
 - easy to build
 - implement basic Boolean algebra operations
- Combine to build more complex circuits
 - memory, adder, multiplier (yhteenlaskupiiri, kertolaskupiiri)
- 1-3 inputs, 1 output

Fig. A.1
- Gate delay (viive)
 - change inputs, new output available after gate delay

19.9.2000 Copyright Teemu Kerola 2000 6

Functionally Complete Set

- Can build all basic gates (and, or, not) from a smaller set of gates
 - and, or, not (trivial!)
 - and, not
 - OR? $A + B = \overline{\overline{A} \cdot \overline{B}}$
 - or, not
 - nand
 - nor

Fig A.2
Fig A.3

19.9.2000 Copyright Teemu Kerola 2000 7

Combinational Circuits ⁽³⁾ (yhdistelmäpiirit)

- Interconnected set of gates
 - change input, wait for gate delays, new output
- Output is Boolean function of input signals
 - m (binary, Boolean) inputs
 - n (binary, Boolean) outputs
- Described in three ways
 - Boolean equations (one for each output)
 - $F = \overline{A}BC + A\overline{B}C + ABC$
 - truth table Table A.3
 - graphical symbols describe implementation with gates and wires Fig A.4

19.9.2000 Copyright Teemu Kerola 2000 8

Simplify Presentation (and Implementation) ⁽³⁾

- Boolean equations
 - Sum of products form (SOP) Fig A.4
 - $F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C$
 - Product of sums form (POS) Fig A.5
 - $F = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + C) \cdot (\overline{A} + \overline{B} + \overline{C})$

Boolean algebra

Which presentation is better?
Fewer gates? Smaller area on chip?
Smaller circuit delay? Faster?

19.9.2000 Copyright Teemu Kerola 2000 9

Algebraic Simplification

- Circuits become too large to handle?
- Use basic identities to simplify Boolean expressions
 - $F = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}C$ Fig A.5
 - $= \overline{A}B + B\overline{C} = B(\overline{A} + \overline{C})$ Fig A.6

- May be difficult to do
- How to do it automatically?
- Build a program to do it "best"?

19.9.2000 Copyright Teemu Kerola 2000 10

Karnaugh Map Squares

- Each square represents complete input value combination (canonical form) order!!
 - adjacent squares differ only in **one** input value (wrap around)

CD:	00	01	11	10
AB:				
00	0000	0001	0011	0010
01	0100	0101	0111	0110
11	1100	1101	1111	1110
10	1000	1001	1011	1010

Square for input value combination $ABCD = 1001$

19.9.2000 Copyright Teemu Kerola 2000 11

Karnaugh Maps


- Represent Boolean function (I.e., circuit) truth table in another way Fig A.7
 - each square is **one product** in sums-of-products (SOP) presentation
 - value is one (1) iff corresponding input values give value 1
 - value is function value for those input values

		00	01	11	10	CD
	00				1	
	01					
	11	1				
	10			1		
AB						

19.9.2000 Copyright Teemu Kerola 2000 12

Karnaugh Map Simplification

- Starting point:
 - Adjacent squares differ only in one input variable value



Adjacent squares have value 1

Input values differ only in one variable

Value of that variable is irrelevant (when all other input variables are fixed to corresponding values for those squares)

Can ignore that variable for those expressions


19.9.2000 Copyright Teemu Kerola 2000 13

Using Karnaugh Maps to Minimize Boolean Functions (6)

Original function $f = \overline{a}bcd + a\overline{b}cd + ab\overline{c}d + abc\overline{d} + \overline{a}bc\overline{d} + \overline{a}b\overline{c}d + \overline{a}b\overline{c}\overline{d} + \overline{a}b\overline{c}d$

Canonical form (now already there)

Karnaugh Map

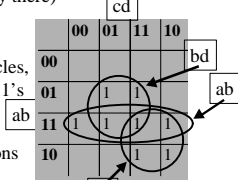

Find smallest number of circles, each with largest number of 1's


Select parameter combinations corresponding to the circles

Get reduced function $f = bd + ac + ab$

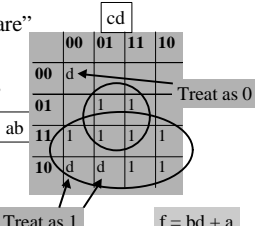19.9.2000 Copyright Teemu Kerola 2000 14

Impossible Input Variable Combinations

- What if some input combinations can never occur?
 - Mark them "don't care" or "d"
 - treat them as 0 or 1, whichever is best
 - more room to optimize



Treat as 0

Treat as 1

$f = bd + a$

19.9.2000 Copyright Teemu Kerola 2000 15


Example: Circuit to add 1 (mod 10) to 4-bit BCD decimal number (4)

5 = 0101
9 = 1001

ABCD

0110 = 6
0000 = 0

WXYZ

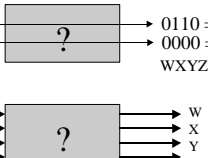

Truth table? Table A.4

Karnaugh maps for W, X, Y and Z? Fig. A.10

19.9.2000 Copyright Teemu Kerola 2000 16

Quine-McKluskey Method

- Another method to minimise Boolean expressions
- Why?
 - Karnaugh maps become complex with 6 input variables
- Quine-McKluskey method
 - tabular method
 - automatically suitable for programming
 - details skipped

19.9.2000 Copyright Teemu Kerola 2000 17

Basic Combinational Circuits

- Building blocks for more complex circuits
 - Multiplexer
 - Encoders/decoder
 - Read-Only-Memory
 - Adder

19.9.2000 Copyright Teemu Kerola 2000 18


Multiplexers ⁽²⁾

- Select one of many possible inputs to output
 - black box Fig A.12
 - simple truth table Tbl A.7
 - implementation Fig A.13
- Each input “line” can be many parallel lines
 - select one of three 16 bit values Fig A.14
 - $C_{0..15}$, $IR_{0..15}$, $ALU_{0..15}$
 - simple extension to one line selection

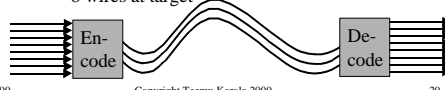19.9.2000 Copyright Teemu Kerola 2000 19

Encoders/Decoders

- Only one of many Encoder input or Decoder output lines can be 1
- Encode the line number as output
 - hopefully less pins (wires) needed this way
 - Example:
 - encode 8 input wires with 3 output pins
 - route 3 wires around the board
 - decode 3 wires back to 8 wires at target Fig A.15



19.9.2000 Copyright Teemu Kerola 2000 20

Read-Only-Memory (ROM) ⁽⁴⁾


- Given input values, get output value
- Consider input as address, output as contents of memory location
- Truth tables for a ROM Table A.8
 - 64 bit ROM
 - 16 words, each 4 bits wide

Mem (7) = 4 Mem (11) = 14

- Implementation with decoder & or gates

19.9.2000 Copyright Teemu Kerola 2000 21

Adders ⁽⁴⁾

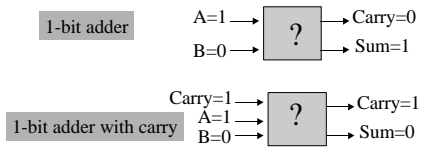

Implementation Table A.9, Fig A.22

Build 4-bit adder from 4 1-bit adders Fig A.21

19.9.2000 Copyright Teemu Kerola 2000 22


Sequential Circuit (sarjalliset piirit)

- Circuit has (modifiable) internal state
- Output of circuit depends (also) on internal state
 - not only from current inputs
 - output = $f(\text{input, state})$
 - new state = $f(\text{input, state})$
- Processor control, registers

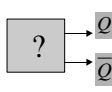19.9.2000 Copyright Teemu Kerola 2000 23

Flip-Flop (kiikku)

- 2 states for Q (0 or 1, true or false)
- 2 outputs Q and \bar{Q}
 - complement values
 - both always available on different pins
- Need to be able to change the state (Q)



19.9.2000 Copyright Teemu Kerola 2000 24

S-R Flip-Flop or S-R Latch (4)

(laituri)

Usually both 0

“Write 1” = “set S=1 for a short time” = “set”

“Write 0” = “set R=1 for a short time” = “reset”

nor (0, 0) = 1
nor (0, 1) = 0
nor (1, 0) = 0
nor (1, 1) = 0

19.9.2000 Copyright Teemu Kerola 2000 25

S-R Latch Stable States (3)

- 1 bit memory (value = value of Q)
- bi-stable, when R=S=0
 - Q=0?
 - Q=1?

nor (0, 0) = 1
nor (0, 1) = 0
nor (1, 0) = 0
nor (1, 1) = 0

19.9.2000 Copyright Teemu Kerola 2000 26

S-R Latch Set (1) and Reset (0) (n)

Write 1: S=0 → 1 → 0

Write 0: R=0 → 1 → 0

nor (0, 0) = 1
nor (0, 1) = 0
nor (1, 0) = 0
nor (1, 1) = 0

19.9.2000 Copyright Teemu Kerola 2000 27

Clocked Flip-Flops

- State change can happen only when clock is 1
 - more control on state changes
- Clocked S-R Flip-Flop [Fig. A.26](#)
- D Flip-Flop [Fig. A.27](#)
 - only one input D
 - D = 1 and CLOCK → write 1
 - D = 0 and CLOCK → write 0
- J-K Flip-Flop [Fig. A.28](#)
 - Toggle Q when J=K=1 [Fig. A.29](#)

19.9.2000 Copyright Teemu Kerola 2000 28

Registers (2)

- Parallel registers
 - read/write [Fig. A.30](#)
 - CPU user registers
 - additional internal registers
- Shift Registers
 - shifts data 1 bit to the right [Fig. A.31](#)
 - serial to parallel?
 - ALU operation?
 - rotate?

19.9.2000 Copyright Teemu Kerola 2000 29

Counters (4)

- Add 1 to stored counter value
- Counter
 - parallel register plus increment circuits
- Ripple counter
 - asynchronous
 - increment least significant bit, and handle “carry” bit as far as needed
- Synchronous counter
 - modify all counter flip-flops simultaneously
 - faster, more complex, more expensive

19.9.2000 Copyright Teemu Kerola 2000 30

Summary

- Boolean Algebra → Gates → Circuits
 - can implement all with NANDs or NORs
 - simplify circuits: Karnaugh, Quine-McKluskey
- Components for CPU design
 - ROM, adder
 - multiplexer, encoder/decoder
 - flip-flop, register, shift register, counter


19.9.2000

Copyright Teemu Kerola 2000

31

-- End of Appendix A: Digital Logic --

Simple processor

 

http://www.gamezero.com/team-0/articles/math_magic/micro/stage4.html

19.9.2000

Copyright Teemu Kerola 2000

32