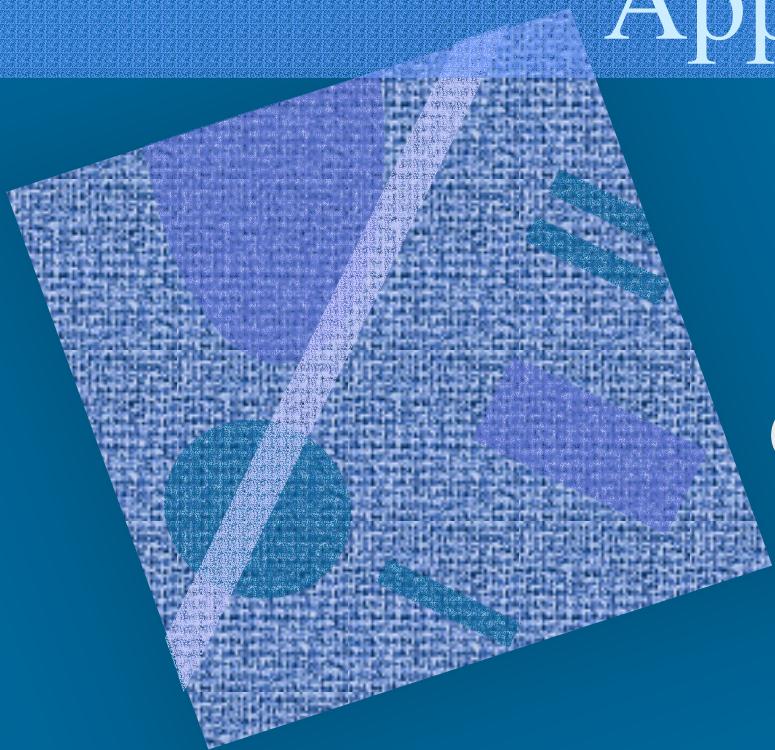


Digital Logic

Appendix A

Boolean Algebra
Gates
Combinatorial Circuits
Sequential Circuits



Boolean Algebra

- George Boole
 - ideas 1854
- Claude Shannon,
 - apply to circuit design, 1938 (piirisuunnittelu)
- Describe digital circuitry function
 - programming language?
- Optimise given circuitry
 - use algebra (Boolean algebra) to manipulate (Boolean) expressions into simpler expressions

Boolean Algebra

(tulo,
yhteenlasku
negaatio)

- Variables: A, B, C
- Values: TRUE (1), FALSE (0)
- Basic logical operations:
 - binary: AND (\bullet), OR (+) $A \bullet B = AB$ $B + C$
 - unary: NOT ($\bar{}$) \bar{A}
- Composite operations, equations
 - precedence: NOT, AND, OR
 - parenthesis $D = A + \bar{B} \bullet C = A + ((\bar{B})C)$

Boolean Algebra

- Other operations

- NAND

- NOR

- Truth tables

- What is the result
of the operation?

Table A.1

		Q
AND		0
		1
		0
P		0
		0
		1
		0
		1

$$A \text{ NAND } B = \text{NOT}(A \text{ AND } B) = \overline{AB}$$

$$A \text{ NOR } B = \text{NOT}(A \text{ OR } B) = \overline{A + B}$$

P	Q	P AND Q
0	0	0
0	1	0
1	0	0
1	1	1

Postulates, Identities in Boolean Algebra

- How can I manipulate expressions?
 - Simple set of rules?
- Basic identities
 - commutative laws
 - distributive laws
 - identity elements
 - inverse elements
 - associative laws
 - DeMorgan's theorem

Table A.2

(vaihdantalait)

(osittelulait)

(identiteetit)


(vasta-alkiot)

(liitääntälait)

(DeMorganin laki)

Gates

(portit)

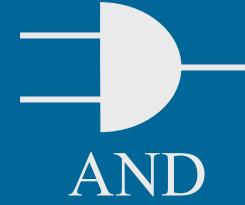- Fundamental building blocks
 - easy to build <http://tech-www.informatik.uni-hamburg.de/applets/cmos/cm OSDemo.html>
 - implement basic Boolean algebra operations
 - Combine to build more complex circuits
 - memory, adder, multiplier
 - 1-3 inputs, 1 output
 - Gate delay
 - change inputs, after gate delay new output available
- [Fig. A.1](#)
- 
- AND
- [\(yhteenlaskupiiri, kertolaskupiiri\)](#)
- AND, OR, NOT, NAND, NOR
- [\(viive\)](#)
- 1 ns? 10 ns? 0.1 ns?


Functionally Complete Set

- Can build all basic gates (“and”, “or”, “not”) from a smaller set of gates

- With “and”, “or”, “not” (trivial!)
 - With “and”, “not”

- “or”?
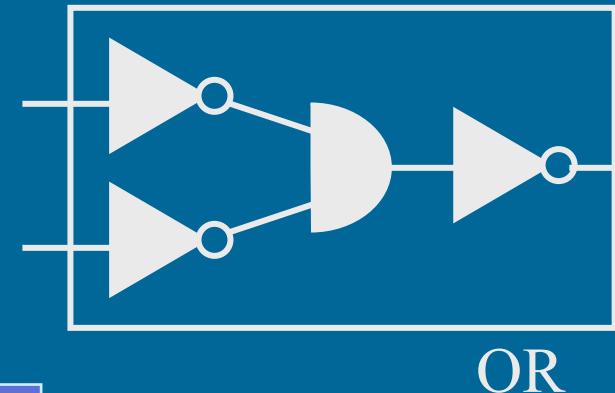
$$A + B = \overline{\overline{A} \bullet \overline{B}}$$



OR

- With “or”, “not”

- With “nand” alone Fig A.2

- With “nor” Fig A.3

Combinational Circuits (3)

(yhdistelmä-
piirit)

- Interconnected set of gates
 - change input, wait for gate delays, new output
- Output is Boolean function of input signals
 - m (binary, Boolean) inputs
 - n (binary, Boolean) outputs
- Described in three ways
 - describe function with *Boolean equations*
(one for each output)
$$F = \overline{ABC} + \overline{ABC} + ABC$$
 - describe function with *truth table* Table A.3
 - describe implementation with graphical symbols for gates and wires Fig A.4

Simplify Presentation (and Implementation) (3)

- Boolean equations
 - Sum of products form (SOP)

$$F = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C}$$

- Product of sums form (POS)

$$F = (A + B + C) \bullet (A + B + \overline{C}) \bullet (\overline{A} + B + C) \\ \bullet (\overline{A} + B + \overline{C}) \bullet (\overline{A} + \overline{B} + \overline{C})$$

Fig A.4

} Boolean
algebra

Fig A.5

Which presentation is better?

Fewer gates? Smaller area on chip?

Smaller circuit delay? Faster?

Algebraic Simplification

- Circuits become too large to handle?
- Use basic identities to simplify Boolean expressions

$$\begin{aligned} F &= \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C} \\ &= \overline{A}B + B\overline{C} = B(\overline{A} + \overline{C}) \end{aligned}$$

Fig A.4

Fig A.6

- May be difficult to do
- How to do it automatically?
- Build a program to do it “best”?

$$\begin{aligned} f &= \overline{a}\overline{b}\overline{c}\overline{d} + \overline{a}\overline{b}c\overline{d} + a\overline{b}\overline{c}\overline{d} + a\overline{b}\overline{c}d \\ &\quad + abcd + abc\overline{d} + a\overline{b}cd + a\overline{b}c\overline{d} \end{aligned}$$

Karnaugh Map Squares

- Each square represents complete input value combination
 - canonical form: each term has each variable once
 - adjacent squares differ only in one input value (wrap around)

Square for input value combination

$$\overline{A}\overline{B}CD = 1001$$


CD:		00	01	11	10
AB	00	0000	0001	0011	0010
	01	0100	0101	0111	0110
AB	11	1100	1101	1111	1110
	10	1000	1001	1011	1010

order!

Karnaugh Maps

- Represent Boolean function (I.e., circuit) truth table in another way
 - each square is **one product** in sums-of-products (SOP) presentation
 - value is **one** (1) iff corresponding input values give value 1, o/w value is “empty”
 - I.e., value is 1 iff function value for those input values is one

Fig A.7

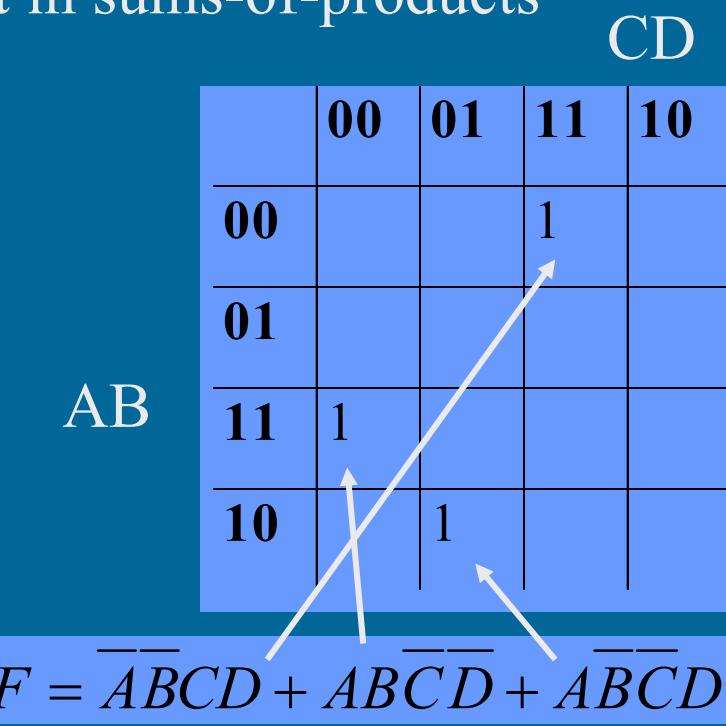

Karnaugh Map Simplification (3)

- Starting point:
 - Adjacent squares differ only in one input variable value

1	1
---	---

Adjacent squares have value 1

C	\bar{C}
-----	-----------

Input values differ only in one variable



Value of that variable is irrelevant
(when all other input variables are fixed
to corresponding values for those squares)



Can ignore that variable for those expressions

Using Karnaugh Maps to Minimize Boolean Functions (8)


Original function

$$f = \overline{ab}\overline{cd} + \overline{a}\overline{b}\overline{c}\overline{d} + \overline{a}\overline{b}\overline{c}\overline{d} + \overline{a}\overline{b}\overline{c}\overline{d}$$
$$+ ab\overline{cd} + ab\overline{c}\overline{d} + a\overline{b}\overline{cd} + a\overline{b}\overline{c}\overline{d}$$

Canonical form (now already there)

Karnaugh Map

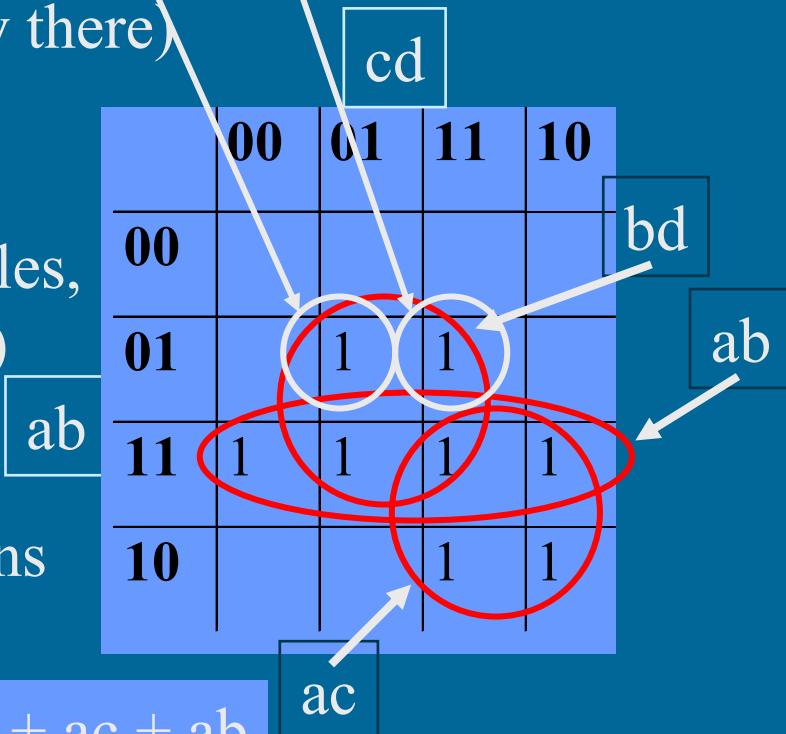Find smallest number of circles,
each with largest number (2^i)
of 1's




Select parameter combinations
corresponding to the circles

Get reduced function $f = bd + ac + ab$

Impossible Input Variable Combinations

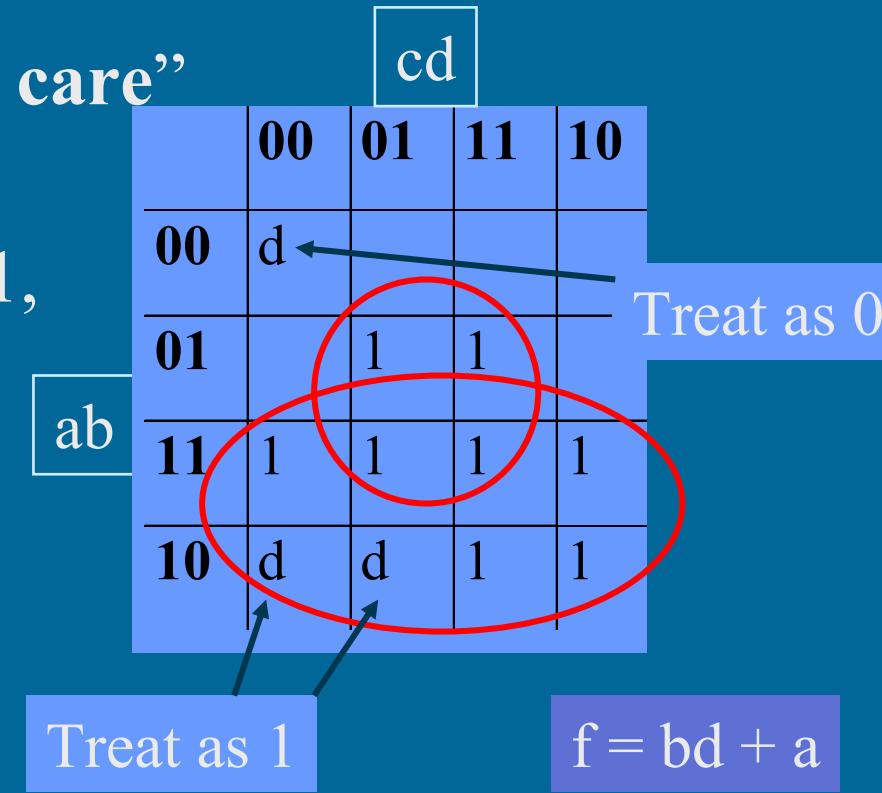- What if some input combinations can never occur?
 - Mark them "don't care" or "d"
 - treat them as 0 or 1, whichever is best
 - more room to optimize



Example: Circuit to add 1 (mod 10) to 4-bit BCD decimal number (4)



Truth table?

Table A.4

Karnaugh maps for W, X, Y and Z?

Fig. A.10

Quine-McKluskey Method

- Another method to minimise Boolean expressions
- Why?
 - Karnaugh maps become complex with 6 input variables
- Quine-McKluskey method
 - tabular method
 - automatically suitable for programming
 - details skipped

Luque Method

- Another method to minimise Boolean expressions
- Based on dividing circle in different ways
- Can be fractally expanded to infinitely many variables
- Interesting, but not part of this course
- Details skipped

See http://www.cs.helsinki.fi/Teemu.Kerola/tikra/artikkelit/d_luque_1.pdf
(September 2003)

Basic Combinational Circuits

- Building blocks for more complex circuits
 - Multiplexer
 - Encoders/decoder
 - Read-Only-Memory
 - Adder

Multiplexers (2)

- Select one of many possible inputs to output
 - black box
 - simple truth table
 - implementation
- Each input/output “line” can be many parallel lines
 - select one of three 16 bit values
 - $C_{0..15}$, $IR_{0..15}$, $ALU_{0..15}$
 - simple extension to one line selection
 - lots of wires, plenty of gates ...

Fig A.12

Tbl A.7

Fig A.13

Fig A.14

Encoders/Decoders

- Only one of many Encoder input or Decoder output lines can be 1
- Encode that line number as output
 - hopefully less pins (wires) needed this way
 - optimise for space, not for time
 - Example:
 - encode 8 input wires with 3 output pins
 - route 3 wires around the board
 - decode 3 wires back to 8 wires at target

Fig A.15



Read-Only-Memory (ROM) (4)

- Given input values, get output value
 - Like multiplexer, but with fixed data
- Consider input as address, output as contents of memory location
- Truth tables for a ROM
 - 64 bit ROM
 - 16 words, each 4 bits wide

Table A.8

Mem (7) = 4

Mem (11) = 14


- Implementation with decoder & or gates

Adders (4)

1-bit adder



1-bit adder with carry

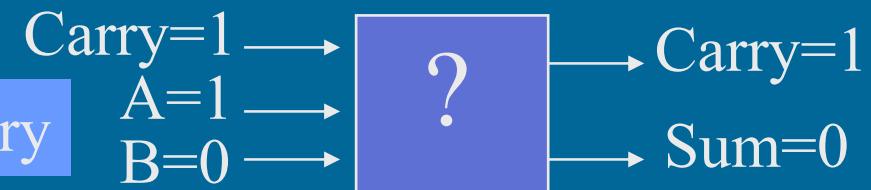


Implementation

Table A.9, Fig A.22

Build a 4-bit adder from four 1-bit adders

Fig A.21

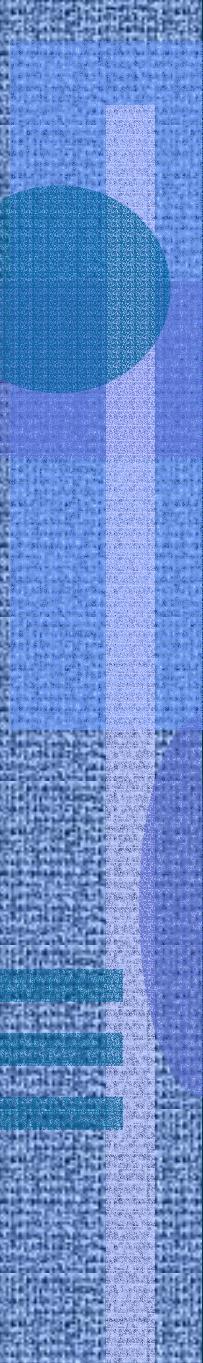

22.9.2003

Copyright Teemu Kerola 2003

2

Sequential Circuit


(sarjalliset piirit)

- Circuit has (modifiable) internal state
- Output of circuit depends (also) on internal state
 - not only from current inputs
 - output = f_o (input, state)
 - new state = f_s (input, state)
- Processor control, registers, memory

Flip-Flop


(kiikku)

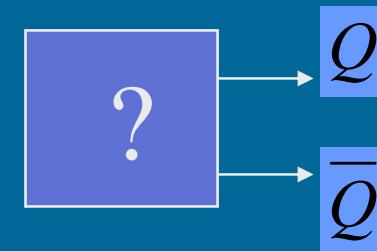- 2 states for Q (0 or 1, true or false)
- 2 outputs Q and \bar{Q}
 - complement values
 - both always available on different pins
- Need to be able to change the state (Q)



S-R Flip-Flop or S-R Latch (3)

(laituri)

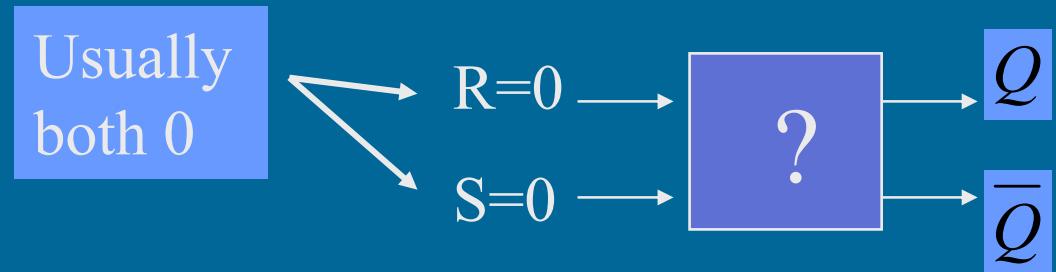


“Write 1” = “set $S=1$ for a short time” = “set”



“Write 0” = “set $R=1$ for a short time” = “reset”

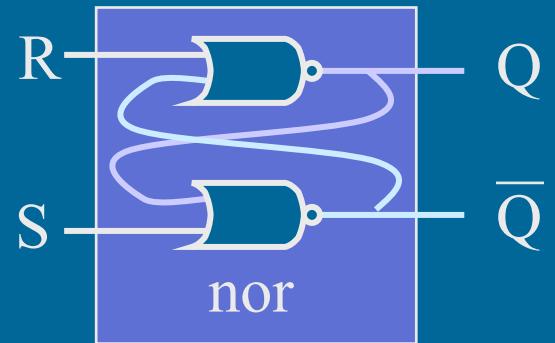
$$\begin{aligned} \text{nor } (0, 0) &= 1 \\ \text{nor } (0, 1) &= 0 \\ \text{nor } (1, 0) &= 0 \\ \text{nor } (1, 1) &= 0 \end{aligned}$$



S-R Latch Stable States (3)

- 1 bit memory (value = value of Q)
- bi-stable, when R=S=0
 - Q=0?
 - Q=1?
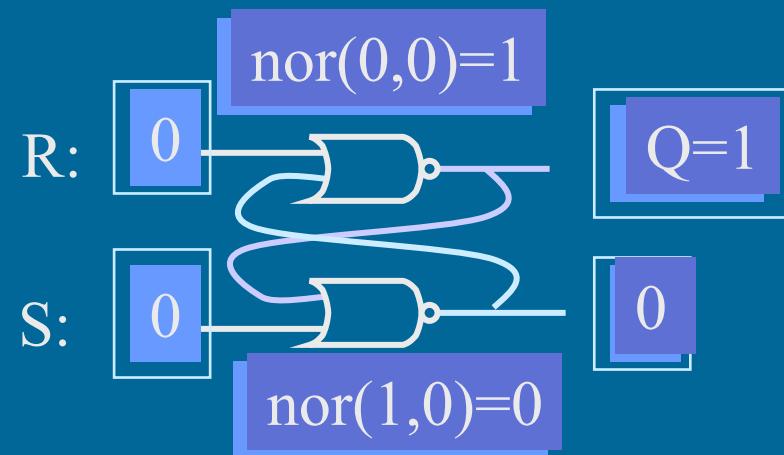
$$\begin{aligned} \text{nor } (0, 0) &= 1 \\ \text{nor } (0, 1) &= 0 \\ \text{nor } (1, 0) &= 0 \\ \text{nor } (1, 1) &= 0 \end{aligned}$$




S-R Latch Set (1) and Reset (0) (n)

Write 1: $S=0 \rightarrow 1 \rightarrow 0$

Write 0: $R=0 \rightarrow 1 \rightarrow 0$
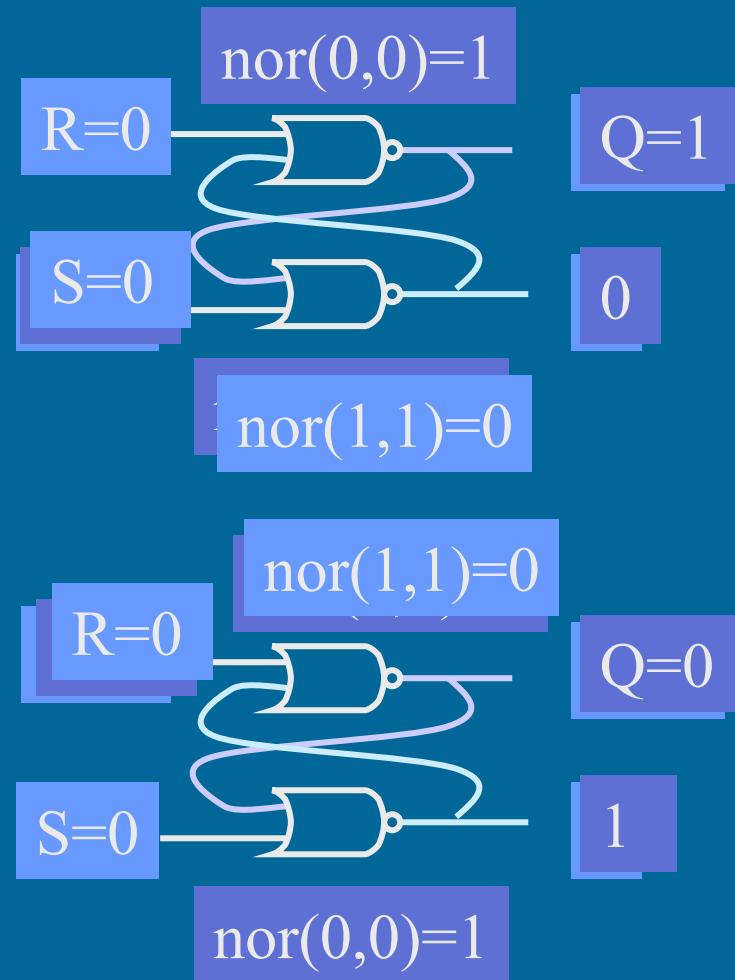
$$\begin{aligned} \text{nor } (0, 0) &= 1 \\ \text{nor } (0, 1) &= 0 \\ \text{nor } (1, 0) &= 0 \\ \text{nor } (1, 1) &= 0 \end{aligned}$$



Clocked Flip-Flops

- State change can happen only when clock is 1
 - more control on state changes
 - Clocked S-R Flip-Flop
 - D Flip-Flop
 - only one input D
 - $D = 1$ and CLOCK \rightarrow write 1
 - $D = 0$ and CLOCK \rightarrow write 0
 - J-K Flip-Flop
 - Toggle Q when $J=K=1$
- Fig. A.26
- Fig. A.27
- Fig. A.28
- Fig. A.29

Registers (2)

- Parallel registers
 - read/write
 - CPU user registers
 - additional internal registers
- Shift Registers
 - shifts data 1 bit to the right
 - serial to parallel?
 - ALU operation?
 - rotate?

Fig. A.30

Fig. A.31

Counters (4)


- Add 1 to stored counter value
- Counter
 - parallel register plus increment circuits
- Ripple counter
 - asynchronous
 - increment least significant bit, and handle “carry” bit as far as needed
- Synchronous counter
 - modify all counter flip-flops simultaneously
 - faster, more complex, more expensive

Summary

- Boolean Algebra → Gates → Circuits
 - can implement all with NANDs or NORs
 - simplify circuits: Karnaugh,
Quine-McCluskey, Luque, ...
- Components for CPU design
 - ROM, adder
 - multiplexer, encoder/decoder
 - flip-flop, register, shift register, counter

-- End of Appendix A: Digital Logic --

Simple processor

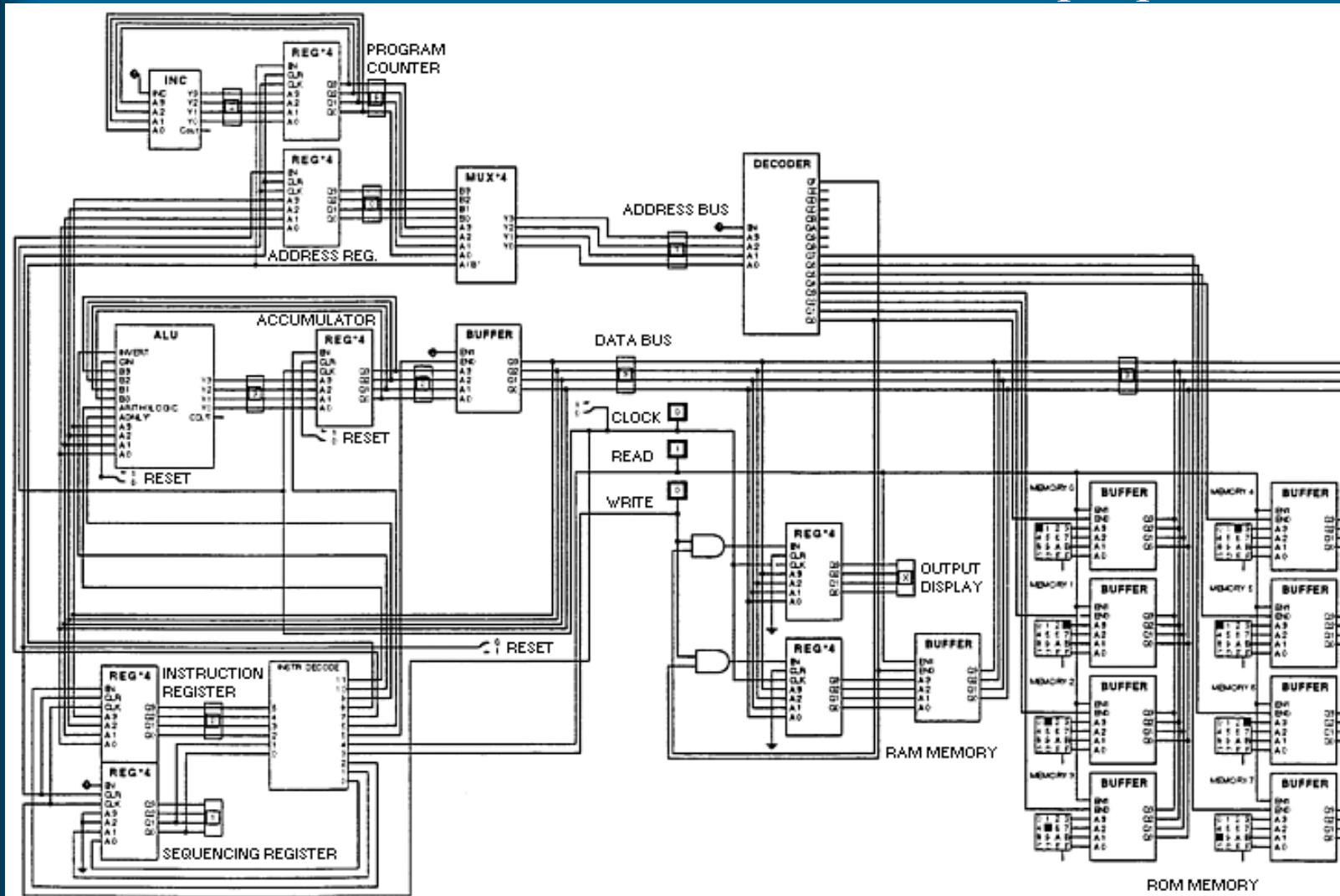

http://www.gamezero.com/team-0/articles/math_magic/micro/stage4.htm