

# Hardwired Control Unit

## Ch 16

Micro-operations  
Controlling Execution  
Hardwired Control

## What is Control <sup>(2)</sup>

- So far, we have shown what happens inside CPU
  - execution of instructions
    - opcodes, addressing modes, registers
    - I/O & memory interface, interrupts
- Now, we show how CPU controls these things that happen
  - how to control what gate or circuit should do at any given time
    - control wires transmit control signals
    - control unit decides values for those signals

# Micro-operations (2)

(mikro-operaatio)

- Basic operations on which more complex instructions are built Fig. 16.1 (Fig. 14.1 [Stal99])
  - each execution phase (e.g., fetch) consists of one or more sequential micro-ops
  - each micro-op executed in one clock cycle in some subsection of the processor circuitry
  - each micro-op specifies what happens in some area of cpu circuitry
  - system cycle time determined by longest micro-op!
- Many micro-ops (for successive instructions) can be executed simultaneously
  - if non-conflicting, independent areas of circuitry

16.10.2003

Copyright Teemu Kerola 2003

3

# Instruction Fetch Cycle (10)

- 4 registers involved Fig. 12.6 (Fig. 11.7 [Stal99])
  - MAR, MBR, PC, IR
- What happens?

Address of next instruction is in PC  
Address (MAR) is placed on address bus  
READ command given to memory  
Result (from memory) appears on data bus  
Data from data bus copied into MBR  
PC incremented by 1  
New instruction moved from MBR to IR  
MBR available for new work

micro-ops?

MAR ← (PC)  
READ

MBR ← (mem)  
PC ← (PC) + 1  
IR ← (MBR)

16.10.2003

Copyright Teemu Kerola 2003

4

# Instruction Fetch Micro-ops (2)

- 4 micro-ops
  - can not change order, can do some ops at the same time
  - s2 must be done after s1
  - s3 can be done simultaneously with s2
  - s4 can be done with s3, but must be done after s2

```
s1: MAR ← (PC), READ
s2: MBR ← (mem)
s3: PC ← (PC) + 1
s4: IR ← (MBR)
```

```
t1: MAR ← (PC)
t2: MBR ← (mem)
    PC ← (PC) + 1
t3: IR ← (MBR)
```

implicit READ

⇒ Need 3 ticks:

assume: mem read in one cycle

# Micro-op Grouping (4)

- Must maintain proper sequence (semantics)
- No conflicts
  - no write to/read from with same register (set?) at the same time
  - each circuitry can be used by only one micro-op at a time
    - E.g., ALU or some bus

```
t1: MAR ← (PC)
t2: MBR ← (mem)
```

```
t2: MBR ← (mem)
t3: IR ← (MBR)
```

```
t2: PC ← (PC) + 1
t3: R1 ← (R1) + (MBR)
```




# Micro-op Types <sup>(4)</sup>

- Transfer data from one reg to another
- Transfer data from reg to external area
  - memory
  - I/O
- Transfer data from external to register
- ALU or logical operation between registers
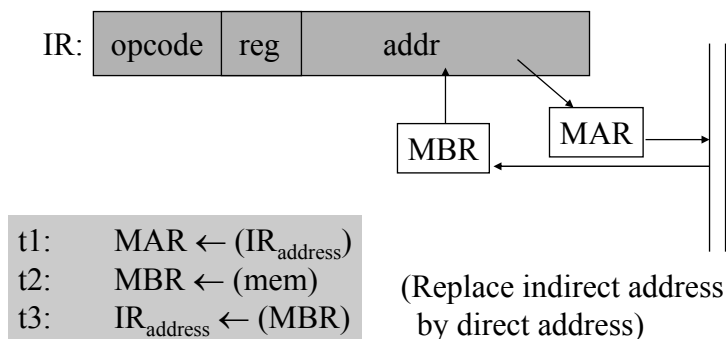
# Indirect Cycle

- Instruction contains address of an operand, instead of direct operand address



# Interrupt Cycle

- After execution cycle, test for interrupts
- If interrupt bits on, then
  - save PC to memory
  - jump to interrupt handler
  - or, find out first correct handler for this type of interrupt and then jump to that (need more micro-ops)
  - context saved by interrupt handler

```

t1:  MBR ← (PC)
t2:  MAR ← save-address
     PC ← routine-address
t3:  mem ← (MBR)
    
```

implicit - just wait?

# Execute Cycle (4)

- Different for each op-code

ADD R1, X

```

t1:  ALU1 ← (R2)
     ALU2 ← (R3)
t2:  ALUout ← "+"
t3:  R1 ← ALUout
    
```

ADD R1, R2, R3

```
t1:  R1 ← (R2) + (R3)
```

JMP LOOP

```
t1:  PC ← (IRaddress)
```

Was this updated in indirect cycle?


BZER R1, LOOP

```
t1:  if ((R1)=0) then
     PC ← (IRaddress)
```

Can this be done in one cycle?
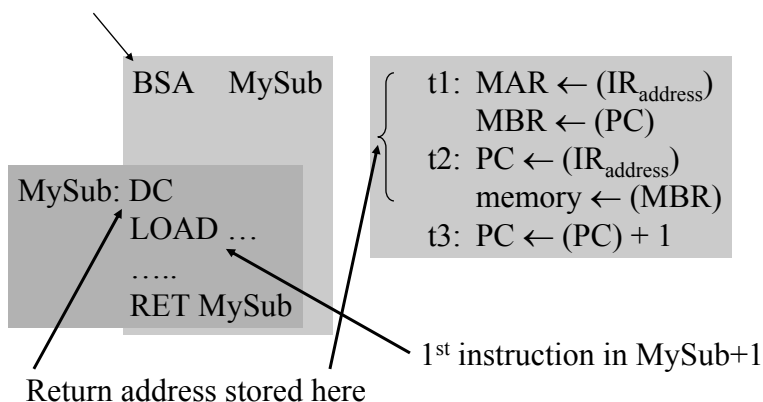
## Execute Cycle (contd) (1)

Branch and Save Address (subroutine call instruction)



16.10.2003

Copyright Teemu Kerola 2003

11

## Instruction Cycle (3)

- Decomposed to micro-ops
- State machine for processor
  - state: execution phase (Fig. 14.3 [Stal99])
  - sub-state: current group of micro-ops executable in one clock cycle (tick) (Fig. 16.3)
- In each sub-state the control signals have specific values dependent
  - on that sub-state (Fig. 14.4 [Stal99])
  - on IR register fields and on flags (Fig. 16.4)
    - including control signals from the bus
    - including values (flags) produced by previous sub-state

16.10.2003

Copyright Teemu Kerola 2003

12

## Control State Machine (2)

- Each state defines current control signal values Control execution
  - determines what happens in next clock cycle
- Current state and current register/flag values determine next state Control sequencing

## Control Signal Types

- Control data flow from one register to another
- Control signals to ALU
  - ALU does also all logical ops
- Control signals to memory or I/O devices
  - via control bus

# Control Signal Example <sup>(5)</sup>

- Accumulator architecture (Fig. 14.5 [Stal99])
- Control signals for given micro-ops cause micro-ops to be executed Fig. 16.5
  - setting  $C_2$  makes value stored in PC to be copied to MAR in next clock cycle Table 16.1
    - $C_2$  controls Input Data Strobe for MAR (see Fig. A.30 for register circuit) (Tbl 14.1 [Stal99])
  - setting  $C_R$  &  $C_5$  makes memory perform a READ and value in data bus copied to MBR in next clock cycle
  - micro-op = collection of control signals?

# Example: Intel 8085 <sup>(5)</sup>

- Introduced 1976
- 3, 5, or 6 MHz, no cache Fig. 16.7
- 8 bit data bus, 16 bit address bus (Fig. 14.7 [Stal99])
  - multiplexed
- One 8-bit accumulator


LDA MyNumber	opcode	address	3 bytes
	0x3A	0x10A5	
OUT #2	opcode	port	2 bytes
	0x2B	0x02	




## Example: i8085 (6)

- Instead of complex data path all data transfers within CPU go via internal bus (Fig. 14.7 [Stal99])  
Fig. 16.7
  - may not be good approach for superscalar pipelined processor - bus should not be bottleneck
- External signals Table 16.2 (Tbl 14.2 [Stal99])
- Each instruction is 1-5 machine cycles
  - one external bus access per machine cycle
- Each machine cycle is 3-5 states
- Each state is one clock cycle (Fig. 14.9 [Stal99])
- Example: OUT instruction Fig. 16.9

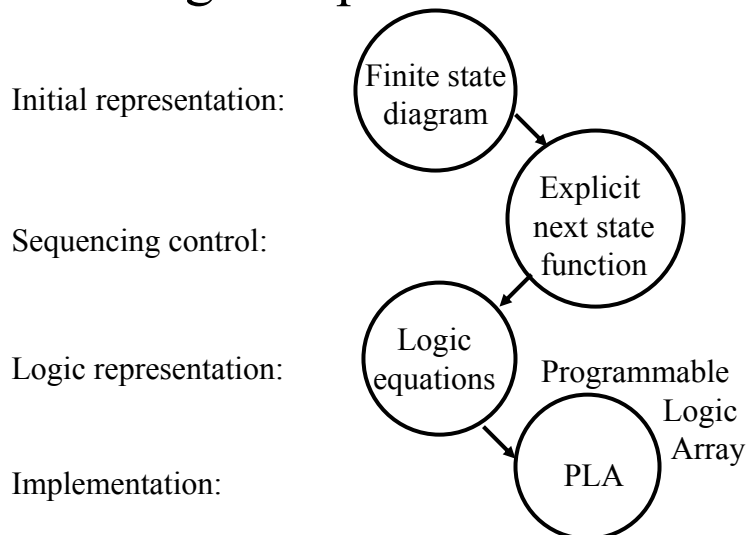
## Hardwired Control Logic Implementation (3)



# Finite State Diagram

 

# Explicit Next State Function

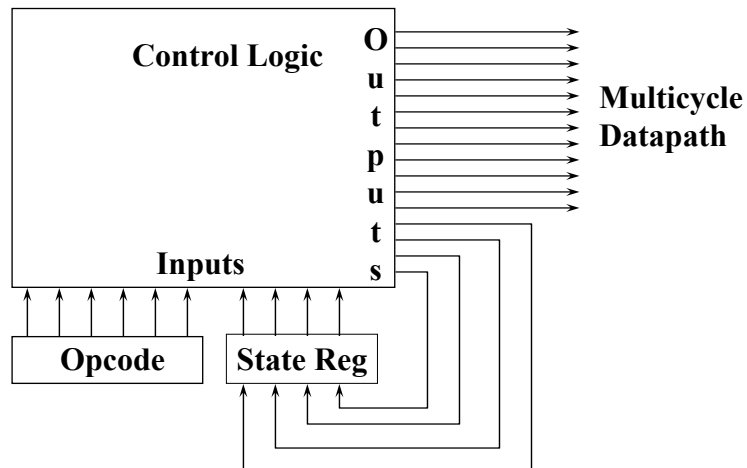

# Logic Equations (2)

## Next state from current state

- State 0 -> State1
- State 1 -> S2, S6, S8, S10
- State 2 -> S5 or ...
- State 3 -> S9 or ...
- State 4 -> State 0
- State 5 -> State 0
- State 6 -> State 7
- State 7 -> State 0
- State 8 -> State 0
- State 9 -> State 0
- State 10 -> State 11
- State 11 -> State 0

## Alternatively, prior state & condition


- S4, S5, S7, S8, S9, S11 -> State0
- \_\_\_\_\_ -> State1
- \_\_\_\_\_ -> State 2
- \_\_\_\_\_ -> State 3
- \_\_\_\_\_ -> State 4
- State2 & op = SW -> State 5
- \_\_\_\_\_ -> State 6
- State 6 -> State 7
- \_\_\_\_\_ -> State 8
- State3 & op = JMP -> State 9
- \_\_\_\_\_ -> State 10
- State 10 -> State 11

# Hardwired Control Logic (3)

- Circuitry becomes very big and complex very soon
  - may be unnecessarily slow
  - simpler is smaller, and thus faster
- Many lines (states) exactly or almost similar
- Have methods to find similar lines (states) and combine them
  - not simple
  - save space, may lose in speed
  - must be redone after any modification
 
## -- End of Chapter 16: Hardwired Control --

HP 9100 Calculator (1968), 20 kg,  
\$5000, 16 regs (data or 14 instructions/reg),  
32Kb ROM, 2208 bit RAM magnetic core memory



Hardwired Control Logic board <http://www.hpmuseum.org/9100cl.jpg>