

Digital Logic Appendix A

Boolean Algebra
Gates
Combinatorial Circuits
Sequential Circuits

6.9.2002 Copyright Teemu Kerola 2002 1

Boolean Algebra

- George Boole
 - ideas 1854
- Claude Shannon,
 - apply to circuit design, 1938 (piirisuunnittelu)
- Describe digital circuitry function
 - programming language?
- Optimise given circuitry
 - use algebra (Boolean algebra) to manipulate (Boolean) expressions into simpler expressions

6.9.2002 Copyright Teemu Kerola 2002 2

Boolean Algebra

- Variables: A, B, C
- Values: TRUE (1), FALSE (0)
- Basic logical operations:
 - binary: AND (\bullet), OR ($+$) $A \bullet B = AB$ $B + C$
 - unary: NOT ($\bar{\quad}$) \bar{A} (ja, tai, ei)
- Composite operations, equations
 - precedence: NOT, AND, OR
 - parenthesis $D = A + \bar{B} \bullet C = A + ((\bar{B})C)$

6.9.2002 Copyright Teemu Kerola 2002 3

Boolean Algebra

- Other operations
 - NAND $A \text{ NAND } B = \text{NOT}(A \text{ AND } B) = \overline{AB}$
 - NOR $A \text{ NOR } B = \text{NOT}(A \text{ OR } B) = \overline{A + B}$
- Truth tables
 - What is the result of the operation?

		Q		
		0	1	
AND	0	0	0	P AND Q
	1	0	1	
P	0	1	0	1

Table A.1 6.9.2002 Copyright Teemu Kerola 2002 4

Postulates, Identities in Boolean Algebra

- How can I manipulate expressions?
 - Simple set of rules?
- Basic identities (Table A.2)
 - commutative laws (vaihdantalait)
 - distributive laws (osittelulait)
 - identity elements (identiteetit)
 - inverse elements (vasta-alkiot)
 - associative laws (liitantalait)
 - DeMorgan's theorem (DeMorganin laki)

6.9.2002 Copyright Teemu Kerola 2002 5


Gates (portit)

- Fundamental building blocks
 - easy to build <http://tech-www.informatik.uni-hamburg.de/applets/cmos/cmosdemo.html>
 - implement basic Boolean algebra operations
- Combine to build more complex circuits
 - memory, adder, multiplier (yhteenlaskupiiri, kertolaskupiiri)
- 1-3 inputs, 1 output AND (Fig. A.1)
- Gate delay (viive)
 - change inputs, new output available after gate delay (1 ns? 10 ns?)

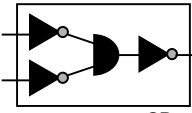6.9.2002 Copyright Teemu Kerola 2002 6

Functionally Complete Set

- Can build all basic gates (“and”, “or”, “not”) from a smaller set of gates
 - With “and”, “or”, “not” (trivial!)
 - With “and”, “not”
 - “or”? $A + B = \overline{\overline{A} \cdot \overline{B}}$
 - With “or”, “not”
 - With “nand” alone Fig A.2
 - With “nor” Fig A.3



OR

6.9.2002 Copyright Teemu Kerola 2002 7

Combinational Circuits ⁽³⁾ (yhdistelmäpiirit)

- Interconnected set of gates
 - change input, wait for gate delays, new output
- Output is Boolean function of input signals
 - m (binary, Boolean) inputs
 - n (binary, Boolean) outputs
- Described in three ways
 - describe function with Boolean equations (one for each output) $F = \overline{A}BC + \overline{A}BC + ABC$
 - describe function with truth table Table A.3
 - describe implementation with graphical symbols for gates and wires Fig A.4

6.9.2002 Copyright Teemu Kerola 2002 8

Simplify Presentation (and Implementation) ⁽³⁾

- Boolean equations
 - Sum of products form (SOP) Fig A.4
 $F = \overline{A}BC + \overline{A}BC + ABC$
 - Product of sums form (POS) Fig A.5
 $F = (A + B + C) \cdot (A + B + \overline{C}) \cdot (\overline{A} + B + C) \cdot (\overline{A} + B + \overline{C})$

Boolean algebra

Which presentation is better?
Fewer gates? Smaller area on chip?
Smaller circuit delay? Faster?

6.9.2002 Copyright Teemu Kerola 2002 9

Algebraic Simplification

- Circuits become too large to handle?
- Use basic identities to simplify Boolean expressions

$$F = \overline{A}BC + \overline{A}BC + ABC$$

$$= \overline{A}B + BC = B(\overline{A} + C)$$

Fig A.5
Fig A.6

- May be difficult to do
- How to do it automatically?
- Build a program to do it “best”?

$$f = \overline{a}bcd + \overline{a}bcd + \overline{a}bcd + \overline{a}bcd + \overline{a}bcd + \overline{a}bcd + \overline{a}bcd + \overline{a}bcd$$

6.9.2002 Copyright Teemu Kerola 2002 10

Karnaugh Map Squares

- Each square represents complete input value combination
 - canonical form: each term has each variable once
 - adjacent squares differ only in one input value (wrap around)

CD:	00	01	11	10	
AB	00	0000	0001	0011	0010
01	0100	0101	0111	0110	
11	1100	1101	1111	1110	
10	1000	1001	1011	1010	

order!!

Square for input value combination
 $\overline{A}BCD = 1001$

6.9.2002 Copyright Teemu Kerola 2002 11

Karnaugh Maps

- Represent Boolean function (I.e., circuit) truth table in another way Fig A.7
 - each square is **one product** in sums-of-products (SOP) presentation
 - value is one (1) iff corresponding input values give value 1, o/w value is “empty”
 - value is 1 if function value for those input values is one

CD	00	01	11	10
00			1	
01				
11	1			
10		1		

AB

$$F = \overline{A}BCD + \overline{A}BCD + \overline{A}BCD$$

6.9.2002 Copyright Teemu Kerola 2002 12

Karnaugh Map Simplification

- Starting point:
 - Adjacent squares differ only in one input variable value



Adjacent squares have value 1
 ↓
 Input values differ only in one variable
 ↓
 Value of that variable is irrelevant
 (when all other input variables are fixed to corresponding values for those squares)
 ↓
 Can ignore that variable for those expressions

Using Karnaugh Maps to Minimize Boolean Functions (6)

Original function $f = \overline{a}bcd + a\overline{b}cd + \overline{a}b\overline{c}d + \overline{a}bc\overline{d} + a\overline{b}c\overline{d} + \overline{a}b\overline{c}\overline{d} + \overline{a}bc\overline{d} + \overline{a}bc\overline{d}$

Canonical form (now already there)

Karnaugh Map


Find smallest number of circles, each with largest number of 1's

Select parameter combinations corresponding to the circles


Get reduced function $f = bd + ac + ab$

Impossible Input Variable Combinations

 - What if some input combinations can never occur?
 - Mark them "don't care" or "d"
 - treat them as 0 or 1, whichever is best
 - more room to optimize



 Example: Circuit to add 1 (mod 10) to 4-bit BCD decimal number (4)



Truth table? Table A.4
 Karnaugh maps for W, X, Y and Z? Fig. A.10

Quine-McKluskey Method

- Another method to minimise Boolean expressions
- Why?
 - Karnaugh maps become complex with 6 input variables
- Quine-McKluskey method
 - tabular method
 - automatically suitable for programming
 - details skipped

Basic Combinational Circuits

- Building blocks for more complex circuits
 - Multiplexer
 - Encoders/decoder
 - Read-Only-Memory
 - Adder

Multiplexers ⁽²⁾

- Select one of many possible inputs to output
 - black box Fig A.12
 - simple truth table Tbl A.7
 - implementation Fig A.13
- Each input/output “line” can be many parallel lines
 - select one of three 16 bit values Fig A.14
 - $C_{0..15}$, $IR_{0..15}$, $ALU_{0..15}$
 - simple extension to one line selection
 - lots of wires, plenty of gates ...

6.9.2002

Copyright Teemu Kerola 2002

19

Encoders/Decoders

- Only one of many Encoder input or Decoder output lines can be 1
- Encode the line number as output
 - hopefully less pins (wires) needed this way
 - optimise for space, not time
 - Example:
 - encode 8 input wires with 3 output pins
 - route 3 wires around the board
 - decode 3 wires back to 8 wires at target Fig A.15



6.9.2002

Copyright Teemu Kerola 2002

20

Read-Only-Memory (ROM) ⁽⁴⁾


- Given input values, get output value
 - Like multiplexer, but with fixed data
 - Consider input as address, output as contents of memory location
 - Truth tables for a ROM Table A.8
 - 64 bit ROM
 - 16 words, each 4 bits wide
- Mem (7) = 4 Mem (11) = 14
- Implementation with decoder & or gates

6.9.2002

Copyright Teemu Kerola 2002

21

Adders ⁽⁴⁾

 

Implementation Table A.9, Fig A.22

Build 4-bit adder from 4 1-bit adders Fig A.21

6.9.2002

Copyright Teemu Kerola 2002

22

Sequential Circuit

(sarjalliset piirit)

- Circuit has (modifiable) internal state
- Output of circuit depends (also) on internal state
 - not only from current inputs
 - output = $f(\text{input}, \text{state})$
 - new state = $f(\text{input}, \text{state})$
- Processor control, registers, memory

6.9.2002

Copyright Teemu Kerola 2002

23

6.9.2002

Copyright Teemu Kerola 2002

24

Flip-Flop (kiikku)

- 2 states for Q (0 or 1, true or false)
- 2 outputs Q and \bar{Q}
 - complement values
 - both always available on different pins
- Need to be able to change the state (Q)

6.9.2002
Copyright Teemu Kerola 2002
25

S-R Flip-Flop or S-R Latch (4) (laituri)

Usually both 0

“Write 1” = “set S=1 for a short time” = “set”

“Write 0” = “set R=1 for a short time” = “reset”

$\text{nor}(0, 0) = 1$
 $\text{nor}(0, 1) = 0$
 $\text{nor}(1, 0) = 0$
 $\text{nor}(1, 1) = 0$

6.9.2002
Copyright Teemu Kerola 2002
26

S-R Latch Stable States (3)

- 1 bit memory (value = value of Q)
- bi-stable, when R=S=0
 - Q=0?
 - Q=1?

$\text{nor}(0, 0) = 1$
 $\text{nor}(0, 1) = 0$
 $\text{nor}(1, 0) = 0$
 $\text{nor}(1, 1) = 0$

6.9.2002
Copyright Teemu Kerola 2002
27

S-R Latch Set (1) and Reset (0) (n)

Write 1: S=0 → 1 → 0

Write 0: R=0 → 1 → 0

$\text{nor}(0, 0) = 1$
 $\text{nor}(0, 1) = 0$
 $\text{nor}(1, 0) = 0$
 $\text{nor}(1, 1) = 0$

6.9.2002
Copyright Teemu Kerola 2002
28

Clocked Flip-Flops

- State change can happen only when clock is 1
 - more control on state changes
- Clocked S-R Flip-Flop Fig. A.26
- D Flip-Flop Fig. A.27
 - only one input D
 - D = 1 and CLOCK → write 1
 - D = 0 and CLOCK → write 0
- J-K Flip-Flop Fig. A.28
 - Toggle Q when J=K=1 Fig. A.29

6.9.2002
Copyright Teemu Kerola 2002
29

Registers (2)

- Parallel registers Fig. A.30
 - read/write
 - CPU user registers
 - additional internal registers
- Shift Registers Fig. A.31
 - shifts data 1 bit to the right
 - serial to parallel?
 - ALU operation?
 - rotate?

6.9.2002
Copyright Teemu Kerola 2002
30

Counters (4)

- Add 1 to stored counter value
- Counter
 - parallel register plus increment circuits
- Ripple counter
 - asynchronous
 - increment least significant bit, and handle “carry” bit as far as needed
- Synchronous counter
 - modify all counter flip-flops simultaneously
 - faster, more complex, more expensive

6.9.2002

Copyright Teemu Kerola 2002

31

Summary

- Boolean Algebra → Gates → Circuits
 - can implement all with NANDs or NORs
 - simplify circuits: Karnaugh, Quine-McKluskey
- Components for CPU design
 - ROM, adder
 - multiplexer, encoder/decoder
 - flip-flop, register, shift register, counter


6.9.2002

Copyright Teemu Kerola 2002

32

-- End of Appendix A: Digital Logic --

Simple processor

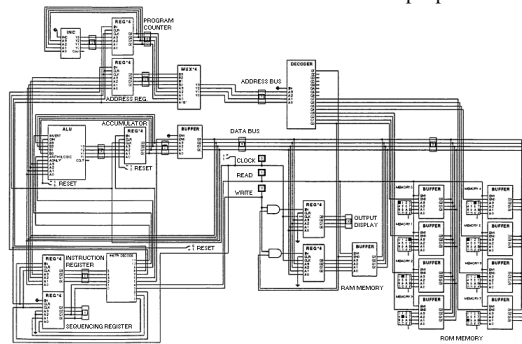

http://www.gamezero.com/team-0/articles/math_magic/micro/stage4.html

6.9.2002

Copyright Teemu Kerola 2002

33